



LAB 4

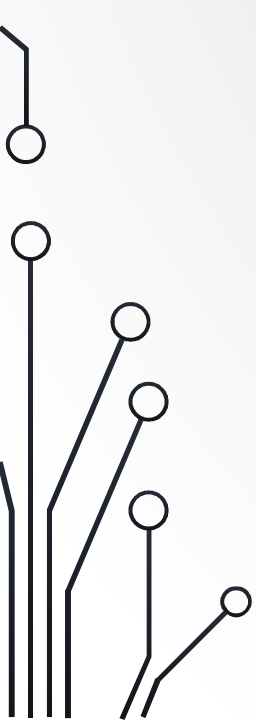
INTRODUCTION TO VHDL


CMP301A: COMPUTER ARCHITECTURE COURSE

EXERPTED FROM DR. ADNAN SHAOUT- *THE UNIVERSITY OF MICHIGAN-
DEARBORN*



OBJECTIVES

 - Declaring New Types.
 - How to initialize Memory.
 - Test-benches.
- 




MEMORY / NEW TYPES ...

- Let's Define the entity of the Ram Block of size 64 byte
- What are the (input/outputs) for this circuit?
- How many bits should represent each Input/Output ?

MEMORY / NEW TYPES ...

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
USE IEEE.numeric_std.all;  
ENTITY ram IS  
  PORT (clk : IN std_logic;  
         we : IN std_logic;  
         address : IN std_logic_vector(5 DOWNTO 0);  
         datain  : IN std_logic_vector(7 DOWNTO 0);  
         dataout : OUT std_logic_vector(7 DOWNTO 0) );  
END ENTITY ram;
```



ARCHITECTURE sync_ram_a **OF** ram **IS**

TYPE ram_type **IS** ARRAY(0 TO 63) of std_logic_vector(7 DOWNT0 0);

SIGNAL ram : ram_type ;

BEGIN

PROCESS(clk) **IS**

BEGIN

IF rising_edge(clk) **THEN**

IF we = '1' **THEN**

 ram(to_integer(unsigned((address))) <= datain;

END IF;

END IF;

END PROCESS;

 dataout <= ram(to_integer(unsigned((address))));

END sync_ram_a;

Defining a new type

```
ARCHITECTURE sync_ram_a OF ram IS  
  TYPE ram_type IS ARRAY(0 TO 63) OF std_logic_vector(7 DOWNT0 0);  
  SIGNAL ram : ram_type ;  
BEGIN  
  PROCESS(clk) IS  
    BEGIN  
      IF rising_edge(clk) THEN  
        IF we = '1' THEN  
          ram(to_integer(unsigned((address))) <= datain;  
        END IF;  
      END IF;  
    END PROCESS;  
    dataout <= ram(to_integer(unsigned((address)))  
END sync_ram_a;
```


Two Dimensional Array

Using the new Type

Remember the numeric Library ?! It contains this functions

What does synchronous mean ?!

Output here is asynchronous

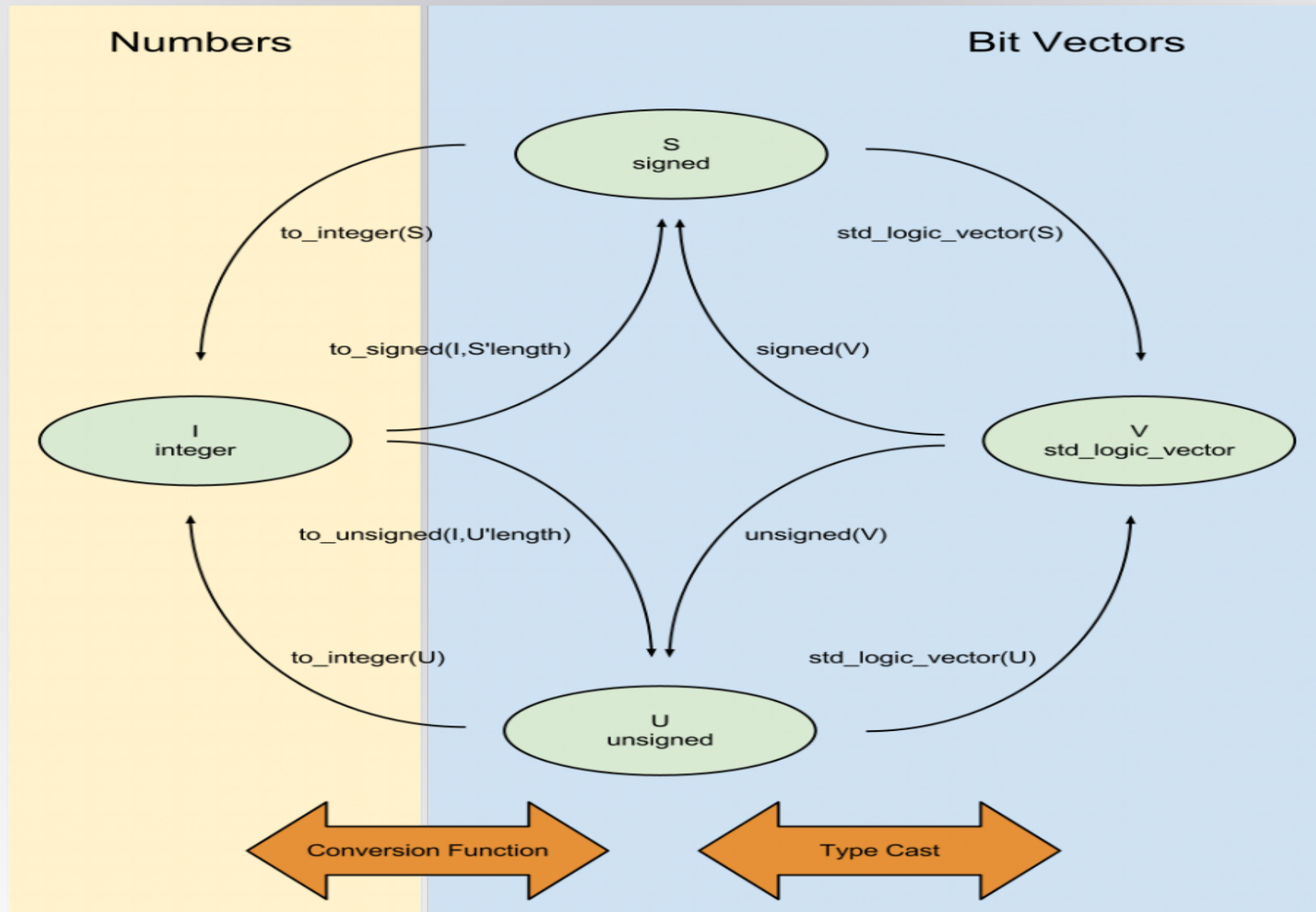

MODELSIM TIME !

∞ INTRO TO VHDL

Architecture course

TEST BENCH EXAMPLE

-- Component under test

ENTITY and2 **IS**

PORT(a,b : IN std_logic;
 z : OUT std_logic);


END and2;

ARCHITECTURE anda **OF** and2 **IS**

BEGIN

 z <= a AND b;

END and_a;

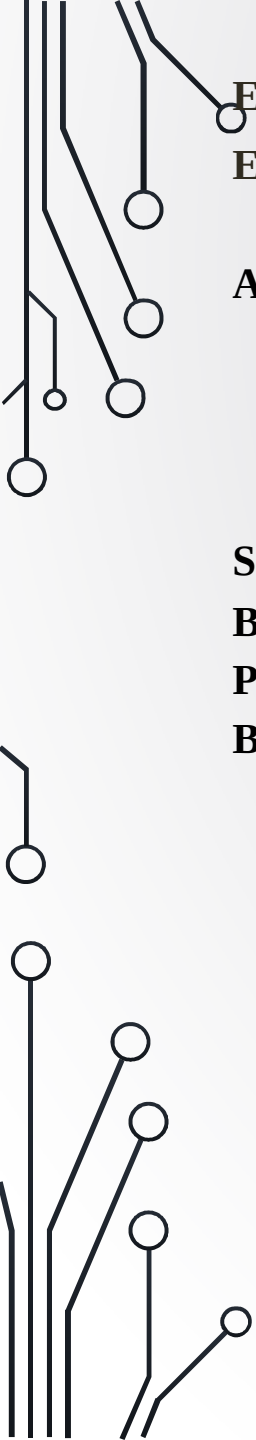

```
ENTITY testbench IS  
END testbench;
```

```
ARCHITECTURE testbench_a OF testbench IS  
    COMPONENT and2 IS  
        PORT ( a,b : IN std_logic; z : OUT std_logic);  
    END COMPONENT;
```

```
SIGNAL testa, testb, testz : std_logic;  
BEGIN  
PROCESS  
BEGIN
```

```
    testa <= '0';
```

```
    testb <= '0';
```

```
    WAIT FOR 10 ns;
```

```
    ASSERT(testz = '0') REPORT "z is not 0 for 00"  
    SEVERITY ERROR;
```

```
    testa <= '0';
```

```
    testb <= '1';
```

```
    WAIT FOR 10 ns;
```

```
    ASSERT(testz = '0') REPORT "z is not 0 for 01"  
    SEVERITY ERROR;
```

```
    testa <= '1';
```

```
    testb <= '0';
```

```
    WAIT FOR 10 ns;
```

```
    ASSERT(testz = '0') REPORT "z is not 0 for 10"  
    SEVERITY ERROR;
```

```
    testa <= '1';
```

```
    testb <= '1';
```

```
    WAIT FOR 10 ns;
```

```
    ASSERT(testz = '1') REPORT "z is not 1 for 11"  
    SEVERITY ERROR;
```

```
WAIT;
```

```
END PROCESS;
```

```
uut: and2 PORT MAP (a => testa, b =>  
testb, z => testz);
```

```
END testbench_a;
```



ENTITY testbench IS
END testbench;

Empty entity

ARCHITECTURE testbench_a OF testbench IS
COMPONENT and2 IS
PORT (a,b : IN std_logic; z : OUT std_logic);
END COMPONENT;

Entity under test

SIGNAL testa, testb, testz : std_logic;

BEGIN

PROCESS

BEGIN

Why used signals instead of variables ?!

Process with No sensitivity list ?!

testa <= '0';

testb <= '0';

Remember Signal takes time to get value

WAIT FOR 10 ns;

ASSERT(testz = '0') REPORT "z is not 0 for 00"

SEVERITY ERROR;

testa <= '0';

testb <= '1';

WAIT FOR 10 ns;

If the condition is true , then it doesn't report

ASSERT(testz = '0') REPORT "z is not 0 for 01"

SEVERITY ERROR;

testa <= '1';

testb <= '1';

WAIT FOR 10 ns;

ASSERT(testz = '1')

SEVERITY ERROR;

testb <= '1';

WAIT FOR 10 ns;

ASSERT(testz = '1') REPORT "z is not 1 for 11"

SEVERITY ERROR;

WAIT;
END PROCESS;

To stop looping forever

uut: and2 PORT MAP (a => testa, b => testb, z => testz);

END testbench_a;

Instantiating the component to be tested

The process and the component works in parallel

Variables will not be seen outside process

Can't We just use a loop instead of writing cases ?

```
PROCESS  
    CONSTANT outCases : std_logic_vector(0 to 3) := "0001";  
BEGIN  
    For i in 0 to 3 Loop  
        test(2 downto 1) <= std_logic_vector(to_unsigned(i,2));  
        WAIT FOR 10 ns;  
        ASSERT(test(0) = outCases(i))    REPORT " Z is not "  
            &std_logic'image(outCases(i))&" zero for "&integer'image(i)  
        SEVERITY ERROR;  
    end loop;  
    WAIT;  
END PROCESS;
```

```

CONSTANT outCases : std_logic_vector(0 to 3) := "0001";
BEGIN
    For i in 0 to 3 Loop
        test(2 downto 1) <= std_logic_vector(to_unsigned(i,2));
        WAIT FOR 10 ns;
        ASSERT(test(0) = outCases(i))    REPORT " Z is not "
            &std_logic'image(outCases(i))&" zero for "&integer'image(i)
        SEVERITY ERROR;
    end loop;
    WAIT;
END PROCESS;

```